
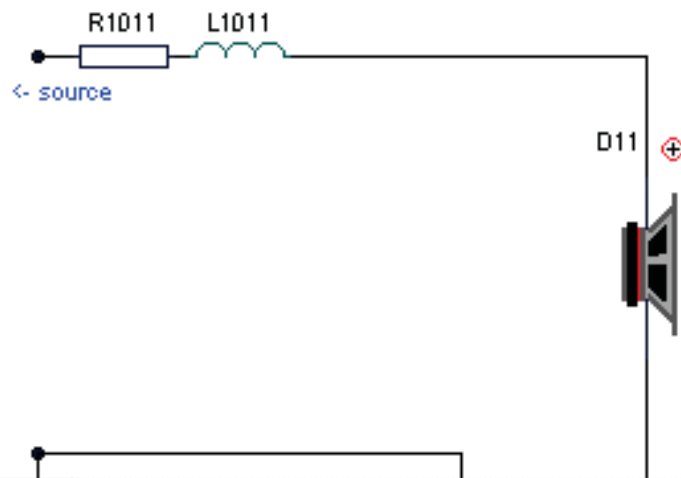


Schematics/overview


R1011 0.300 ohm
L1011 1.000 mH

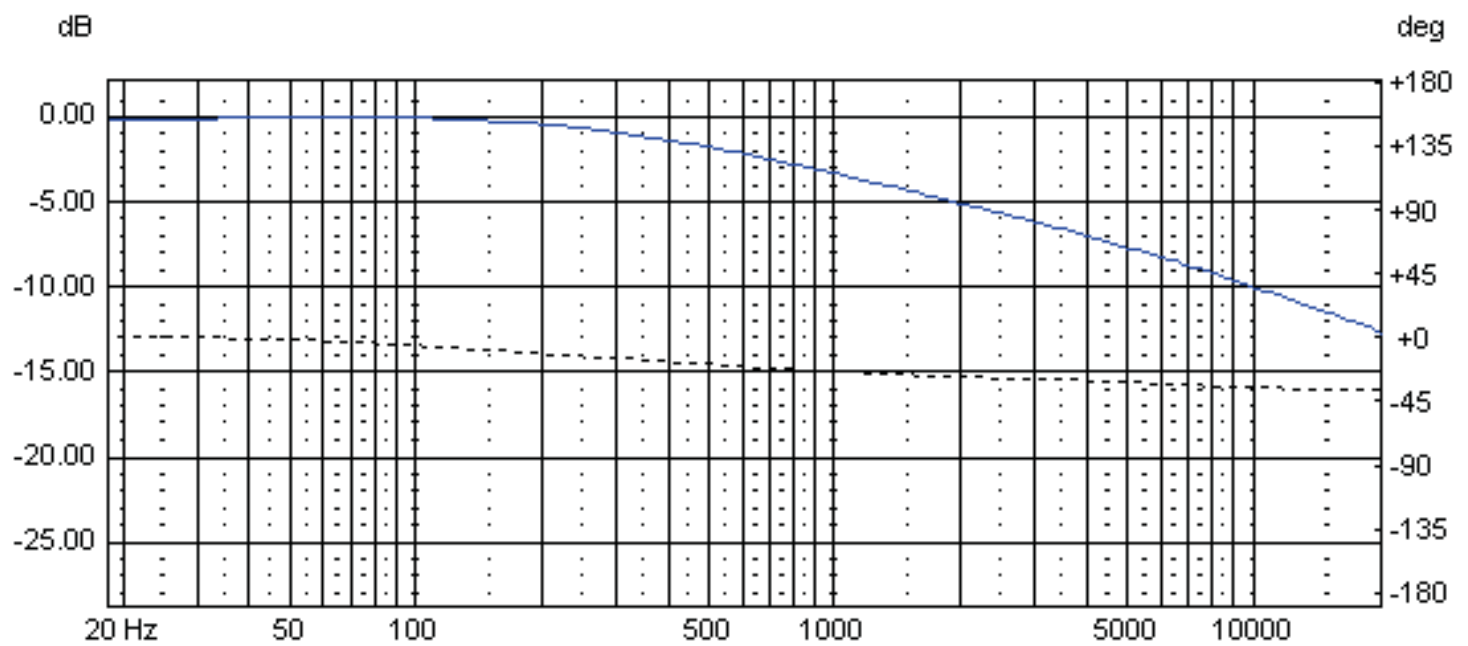

Net 1 gain



Summed frequency response

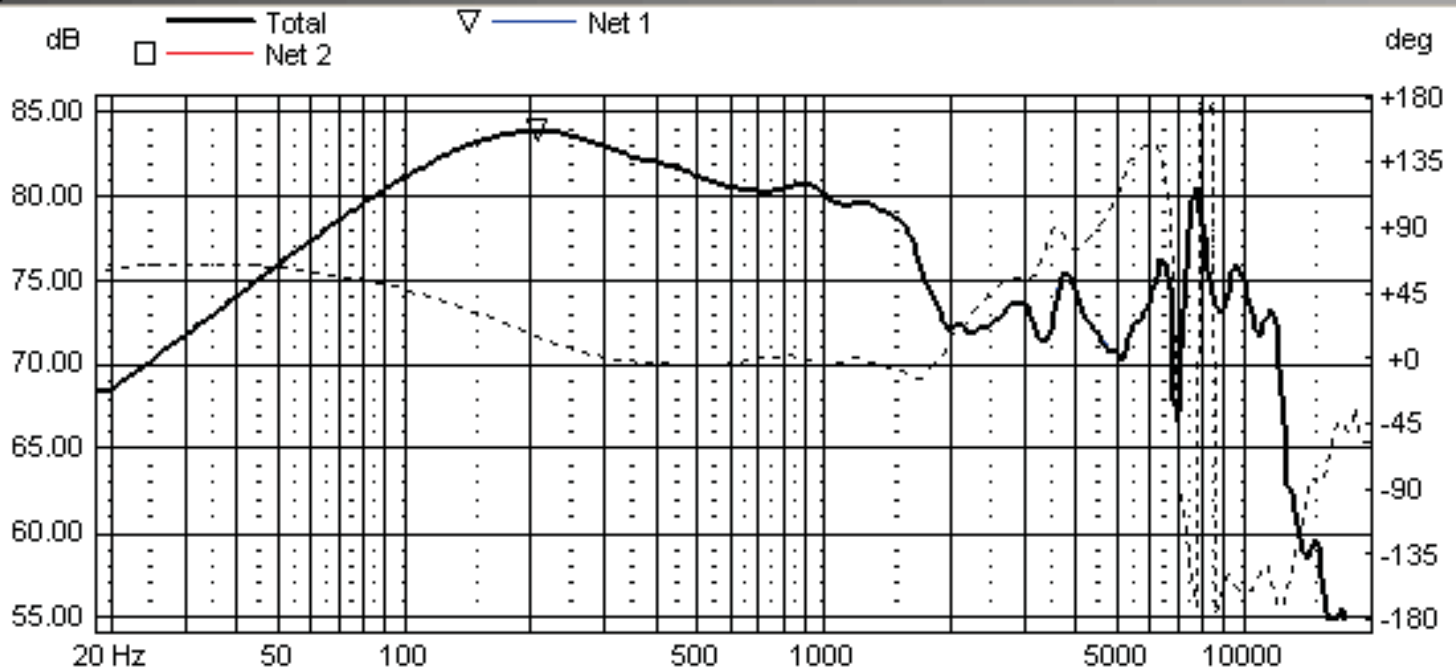

MIT OpenCourseWare
<http://ocw.mit.edu>

Audio and Speaker Electronics
Spring 2007

For information about citing these materials or our Terms of Use, visit: <http://ocw.mit.edu/terms>.